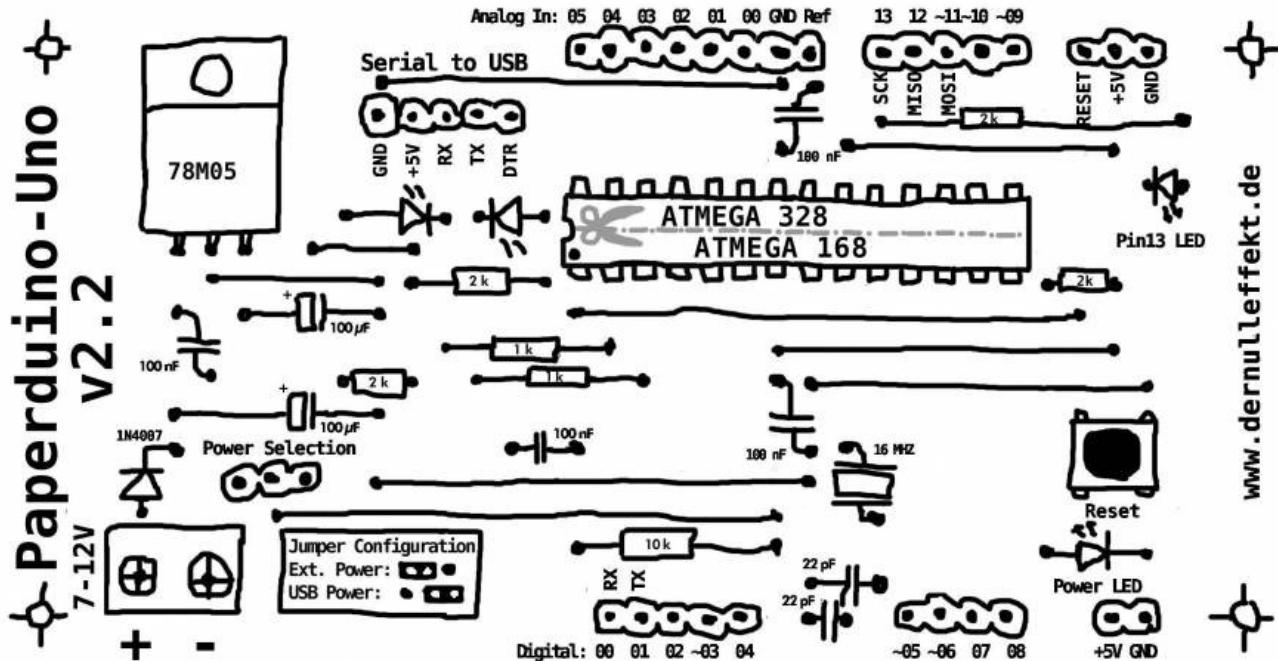


Paperduino-Uno



Parts:

- 1x Atmega 328
- 4x low current LEDs 3mm
- 1x voltage converter 78M05
- 1x crystal 16MHz
- 2x electrolytic capacitor 100 μ F
- 4x capacitor 100nF
- 2x capacitor 22pF
- 1x diode 1N4007
- 7x resistor:
 - 4x 2k0hm, 2x 1k0hm, 1x 10k0hm
- 1x reset button
- 2x jumper